

# Problem Set 9 - LV 141.A55 QISS - 30.5.2016

## 1. Persistent-current qubit

The persistent-current qubit consists of a loop containing three Josephson junctions. Two junctions are equal and the third is by a factor  $\alpha$  smaller. Therefore its Josephson energy is  $\alpha E_J$  and its charging energy  $E_c/\alpha$ .

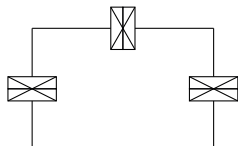


Figure 1: Persistent-current qubit

(a)

$$I_1 = I_0 \sin(\varphi_1) + C\dot{V}_1 = I_0 \sin(\varphi_1) + C \frac{\phi_0}{2\pi} \ddot{\varphi}_1$$

Similar equations hold for the other two junctions. Note the the phase difference of the third junction is  $\varphi_2 - \varphi_1 + 2\pi\phi_{ext}/\phi_0$

$$I_1 = I_3 = -I_2$$

Find the Lagrange function

$$\mathcal{L}(\varphi_1, \varphi_2, \dot{\varphi}_1, \dot{\varphi}_2)$$

and express it in terms of  $E_J, E_c, \alpha, \phi_{ext}$

Show that the Lagrange equations

$$\frac{d}{dt} \left\{ \frac{\partial \mathcal{L}}{\partial \dot{\varphi}_i} \right\} - \frac{\partial \mathcal{L}}{\partial \varphi_i} = 0$$

reproduce the Kirchhoff equations.

(b) Find the canonical conjugate variables  $q_i$  with

$$q_i = \frac{\partial \mathcal{L}}{\partial \dot{\varphi}_i}$$

and express the variables  $\dot{\varphi}_i$  in terms of these new conjugate variables.

(c) Find the Hamilton function by doing a Legendre transformation

$$\mathcal{H}(\varphi_1, \varphi_2, q_1, q_2) = \dot{\varphi}_1 q_1 + \dot{\varphi}_2 q_2 - \mathcal{L}$$

Verify your result by making sure that the canonical equations reproduce the initial Kirchhoff equations.

$$\dot{\varphi}_i = \frac{\partial \mathcal{H}}{\partial q_i} \quad \dot{q}_i = -\frac{\partial \mathcal{H}}{\partial \varphi_i}$$