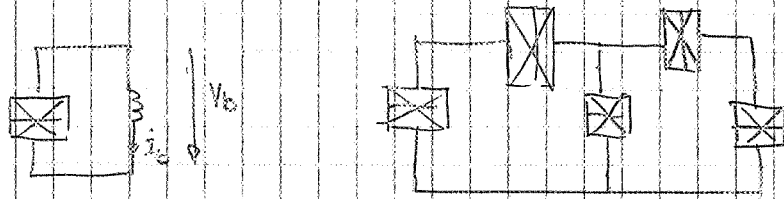


quantizing superconducting circuits

circuit made up of capacitors, inductors,
Josephson junctions



branch currents
branch voltage

i_b
 v_b

Kirchhoff's laws

$$\sum_{\text{node}} i_b = 0$$

$$\sum_{\text{loop}} v_b = 0$$

procedure to find Hamiltonian

write Lagrange function

$$\mathcal{L}(q_1, \dots, q_n, \dot{q}_1, \dots, \dot{q}_n) = T - V$$

Lagrange's equations

$$\frac{d}{dt} \left(\frac{\partial \mathcal{L}}{\partial \dot{q}_i} \right) - \frac{\partial \mathcal{L}}{\partial q_i} = 0$$

- conjugate momentum $p_i(q, \dot{q}_i, t) = \frac{\partial \mathcal{L}}{\partial \dot{q}_i}$
- insert the equations to find \dot{q}_i
- find Hamilton function with a Legendre transformation

$$\begin{aligned} \mathcal{H}(q_i, p_i, t) &= \sum_i \dot{q}_i \frac{\partial \mathcal{L}}{\partial \dot{q}_i} - \mathcal{L} \\ &= \sum_i q_i p_i - \mathcal{L} \end{aligned}$$

Hamilton's equations

$$\dot{p}_i = - \frac{\partial \mathcal{H}}{\partial q_i} \quad \dot{q}_i = \frac{\partial \mathcal{H}}{\partial p_i}$$

- replace variables by operators

$$\begin{aligned} q_i &\rightarrow \hat{q}_i \\ p_i &\rightarrow \hat{p}_i \\ \mathcal{H} &\rightarrow \hat{\mathcal{H}} \quad \text{Hamiltonian} \end{aligned} \quad [\hat{q}_i, \hat{p}_i] = i \hbar$$

Note: Circuit has not unique Hamiltonian depends on representation

recipe to directly find Hamiltonian

- chose one node as ground
- define a loop-free spanning tree
each node is linked to ground
by one and only one path
- define node voltage V_n as
the sum of branch voltages V_b to ground
- define node current i_n as the
current flowing to the node by the
capacitors only


dynamical variables

$$\text{node flux } \phi_n = \int_{-\infty}^+ V_n(\tau) d\tau$$

$$\text{node charge } q_n = \int_{-\infty}^+ i_n(\tau) d\tau$$


Using Kirchhoff's laws, express branch
flux/charge as a linear combination of
node variables

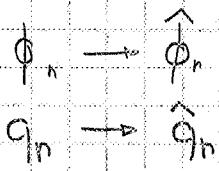- sum energies of all branches to get
Hamiltonian function



$$[\hat{\phi}_y, \hat{q}_m] = i\hbar S_{ym}$$

1st example: LC oscillator

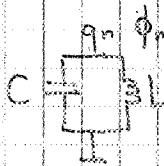

$$i_c = C \frac{d}{dt} v_c \quad \frac{d\phi}{dt} = v_c = v_L$$

Kirchhoff: $i_c + i_L = 0 \quad v_c = v_L$

$$\phi_n = \int v dt = L i_L = L I$$

$$q_n = \int i_c dt = C U$$

$$\mathcal{L}(q, \dot{q}) = \frac{q^2}{2C} - \frac{L}{2} \dot{q}^2$$

$$0 = \frac{d}{dt} \left(\frac{\partial \mathcal{L}}{\partial \dot{q}} \right) - \frac{\partial \mathcal{L}}{\partial q} = -\frac{d}{dt} (L \dot{q}) + \frac{q}{C} - L \ddot{q} - \frac{1}{C} q$$

$$\mathcal{H}(q, \dot{q}) = \frac{1}{2} \frac{q^2}{C} + \frac{1}{2} \frac{\dot{q}^2}{L}$$

$$\hat{\mathcal{H}}(\hat{q}, \hat{\phi}) = \frac{1}{2} \frac{\hat{q}^2}{C} + \frac{1}{2} \frac{\hat{\phi}^2}{L}$$

harmonic oscillator

$$[\hat{q}, \hat{\phi}] = i\hbar$$

$$\hat{q} = \sqrt{\frac{\hbar}{2Z_c}} (a^\dagger + a)$$

$$\hat{\phi} = i \sqrt{\frac{\hbar Z_c}{2}} (a^\dagger - a)$$


$$\hat{a} = \frac{1}{\sqrt{\hbar(2+Z_c)}} (Z_c \hat{q} + i \hat{\phi})$$

$$\hat{a}^\dagger = \frac{1}{\sqrt{\hbar(2+Z_c)}} (Z_c \hat{q} - i \hat{\phi})$$

$$\hat{\mathcal{H}} = \hbar\omega \left(a^\dagger a + \frac{1}{2} \right)$$

$$Z_c = \sqrt{\frac{L}{C}}$$

RF-SQUID

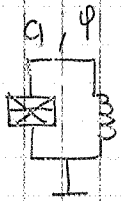

$$\mathcal{H}(q, \phi) = \mathcal{H}_{\text{ind}} + \mathcal{H}_{\text{JJ}}$$

$$\mathcal{H}_{\text{ind}} = \frac{\phi^2}{2L}$$

$$\mathcal{H}_{\text{JJ}} = \frac{q^2}{2C} - E_J \cos(\phi)$$

$$V_{\text{JJ}} = \frac{\phi_0}{2\pi} \delta'$$

$$\phi = \int_{\phi_0}^{\phi} V_{\text{JJ}} d\tau$$


$$\phi_{\text{ext}} = \int v = \phi - \underbrace{\int V_{\text{JJ}} d\tau}_{\frac{\phi_0}{2\pi} \delta}$$

$$\mathcal{H} = \frac{q^2}{2C} + \frac{\phi^2}{2L} - E_J \cdot \cos\left(\frac{2\pi}{\phi_0} (\phi - \phi_{\text{ext}})\right)$$

problem has 2 parameters

$$E_J/E_C \quad \frac{L_J}{L}$$

no analytical solution

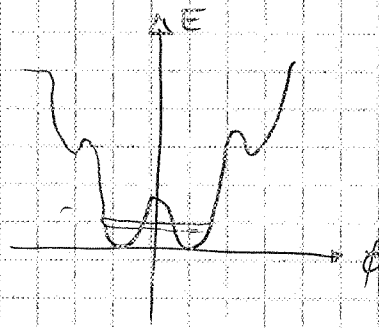

problem: qubit very sensitive to flux noise

Slides

Phase Qubit



current biased junction

$$\mathcal{H} = \frac{q^2}{2C} - I\phi - I\phi_0 \cos\left(\phi - \frac{2\pi}{\phi_0}\right)$$

$$S = 2\pi \frac{\phi}{\phi_0} \quad p = 2eq$$

$$\mathcal{H} = 4E_C p^2 - I\phi_0 S - I\phi_0 \cos(S)$$

$$[S, p] = i$$

for $I \approx I_0$

$$U(S) = \phi_0 (I_0 - I) (S - \pi/2) - \frac{I_0 \phi_0}{2\pi} (S - \pi/2)^3$$

$$\omega_p = \frac{1}{\sqrt{L_J C}} = \frac{1}{\sqrt{L_J C}} \left(1 - (I/I_0)^2\right)^{1/4}$$